

Diodos

Alumno:


■ Resultados

Ejercicios de Simulación

1.2.

V_{ent}	V_d	I_d
3		
2		
1		
0		
-1		
-2		
-3		
-4		
-5		
-6		
-7		
-8		
-9		
-10		
-11		
-12		
-13		
-14		
-15		

1.3.

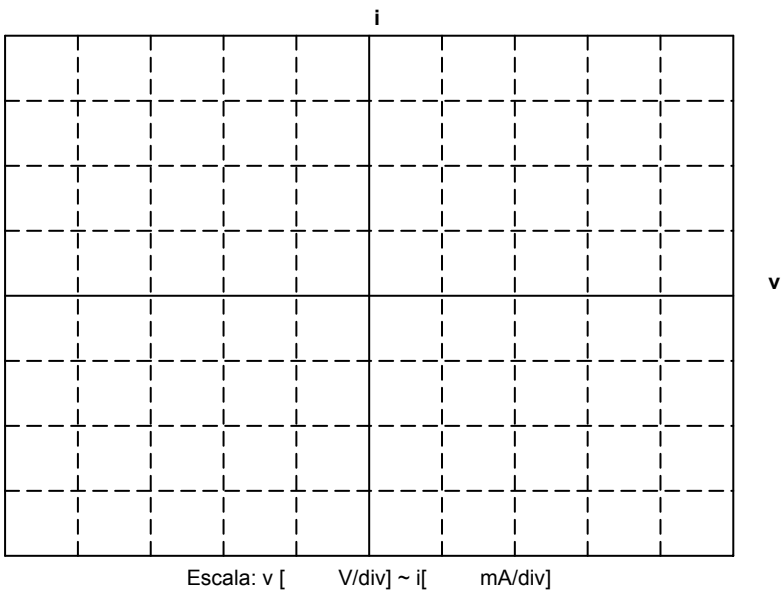

Escala: v [V/div] ~ i [mA/div]

1.4. ~1.5.


V_J	r_d

1.6. ~1.7.

V_B	r_B

Ejercicios de Laboratorio

1.3.

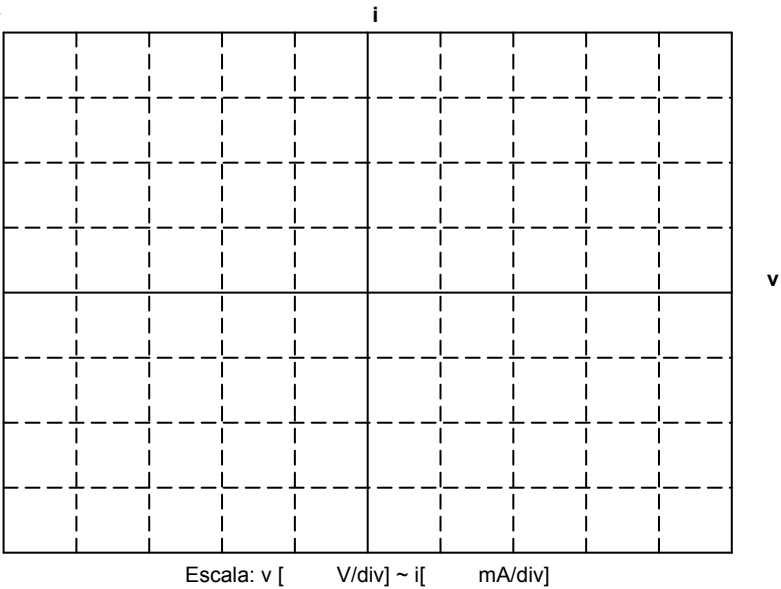

1.4.~1.5.

V _J	V _B